

Tasha Asyiqin, Sophia Godfrey, Mikael Pineda, and Diego Rufino

ECGR 2254

10/17/2022

Robert Cox

Project 1

Problem 1

1aa. Determining the differential equation requires to do KVL. This resulted in:

$$-V_s + V_L + V_R$$

When converting each voltage to its respected conversion, L was then divided on all sides, resulting in the following steps:

$$V_s = L \left(\frac{di}{dt} \right) + IR$$

$$\frac{V_s}{L} = \frac{di}{dt} + \frac{IR}{L}$$

$$\frac{480\sqrt{2}\cos(120\pi)}{0.045} = \frac{di}{dt} + \frac{0.1}{0.0045} * I$$

1ab & 1ac. The following steps show how the steady-state solution of the differential equation was solved:

a. b) $y_{ss}(t) = |B| \cos(2\pi 60t + 0^\circ) = \text{Real}\{ |B| e^{j0^\circ} e^{j2\pi 60t} \}$

$$\frac{d}{dt} + 22.2 \pm = \frac{480\sqrt{2}}{0.0045} \cos(120\pi t) \Rightarrow \frac{d}{dt} (B e^{j2\pi 60t}) + 22.2 (B e^{j2\pi 60t}) = \frac{480\sqrt{2}}{0.0045} e^{j0^\circ} e^{j2\pi 60t}$$

$$\frac{j2\pi 60 + 22.2}{j2\pi 60 + 22.2} (B e^{j2\pi 60t}) = \frac{480\sqrt{2}}{0.0045} e^{j0^\circ} e^{j2\pi 60t} = 150,849.45$$

$$|B| = \frac{150,849.45}{\sqrt{(22.2)^2 + (120\pi)^2}} = 399.45 \angle B = 0^\circ - \tan^{-1}\left(\frac{120\pi}{22.2}\right) = 0 - 86.63^\circ = -86.63^\circ$$

$399.45 \cos(2\pi 60t - 86.63^\circ)$ a. l) 399.45

1ba. When transforming into the form of transient solution and steady-state solution, it results in:

$$V_c(t) = C e^{-\frac{t}{\tau}} + |B| \cos(2\pi 60t + B^\circ)$$

Next was to calculate Δt , $\Delta t / 100$, and ϕ .

1b. a) $V_c(t) = (e^{-t/\tau} + |B| \cos(2\pi 60t + \angle B))$

$$\Delta t \angle (5\pi - 15)(0.045) = 0.255 \quad \Delta t \angle T = \frac{2\pi}{2\pi 60} = 0.017 \text{ secs}$$

$$\Delta t \angle \frac{0.017}{100} = 0.00225 \text{ secs} \quad \Delta t \angle \frac{0.017}{100} = 0.00017 \text{ secs}$$

$$\tau = \frac{1}{R} = 0.045$$

1bb. Plug in both choices of the transient response and the steady-state response for finding t_{end} :

1b. b) Choice 1: $t_{\text{end}} = 7\tau = 7(0.045) = 0.315 \text{ secs}$ Choice 2: $t_{\text{end}} = 2T = 0.034 \text{ secs}$

$t = [0; \Delta t; 7 \cdot \tan]$

The larger result must be picked in order to see the characteristics of the solution.

1bc. Using what the approximation is for dy/dt , the following steps were taken to find the discretized equation:

Handwritten derivation of the discretized equation for current i_L :

$$\frac{di_L}{dt} \approx \frac{i_L(t+\Delta t) - i_L(t)}{\Delta t}$$

$$V_s(t) = V_c(t) + R \left[\frac{i_L(t+\Delta t) - i_L(t)}{\Delta t} \right]$$

$$V_c(t+\Delta t) = f(V_c(t), V_s(t)) = V_c(t) \left(1 - \frac{R\Delta t}{L} \right) + V_s(t) \left(\frac{R\Delta t}{L} \right)$$

$$V_c(t+\Delta t) = V_s(t) \left[\frac{R\Delta t}{L} \right] + V_c(t) \left[1 - \frac{R\Delta t}{L} \right]$$

$$t = n\Delta t \quad V_c(n\Delta t + \Delta t) = V_c(n\Delta t)$$

$$V_c(n+1) = V_s(n) a + V_c(n) b$$

Entering into MATLAB, the current after $t = 0$ and plotting the graph was made:

```
% PROJECT 1
% part A and B
clear all
% values for circuit
Ls = 0.0045;
R1s = 0.1;
phi = deg2rad(0);

% finding time variables
omega = 2*pi*60;
T = (2*pi)/omega;
tau = Ls/R1s;

delta_t = tau/100;
t = [0:delta_t:7*tau];

% defining x & y
v_s = (480*sqrt(2)/.1)*cos(omega*t - phi);
v_c = [];
v_c_0 = 0;


a = delta_t/tau;
b = (1-(a));

for n = 1:length(t)-1
    if n == 1
        v_c = v_c_0;
    end
    v_c(n+1) = a*v_s(n)+b*v_c(n);
end

figure(1);
plot(t,v_c);
title('Current over time');
xlabel('Time: sec');
ylabel('Current (amps)');
```


1bd. 0 degrees = 400, 45 degrees = 640, 90 degrees = 733.5, 135 degrees = 631, & 180 degrees = 410. I chose 90 degrees.

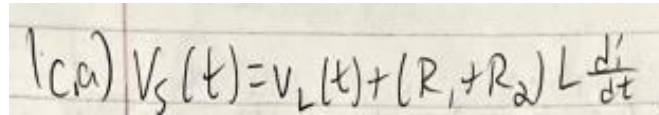1ca. This was the finding differential equation.



$$1ca) V_s(t) = v_L(t) + (R_1 + R_2) L \frac{di}{dt}$$

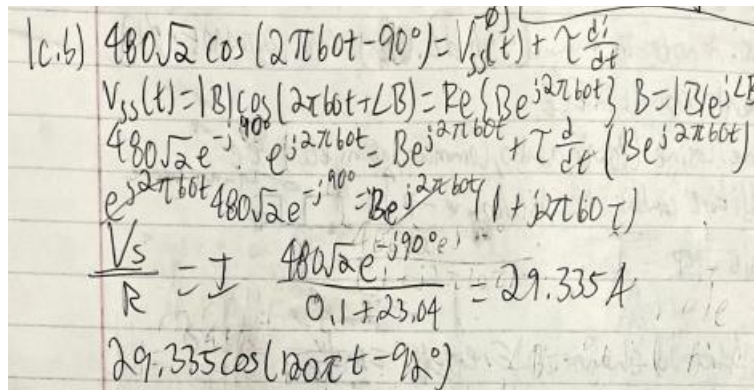1cb. These were the steps to find the steady-state solution, using the finding value of phi.



$$\begin{aligned}
 1cb) \quad & 480\sqrt{2} \cos(2\pi 60t - 90^\circ) = v_{ss}(t) + L \frac{di}{dt} \\
 & v_{ss}(t) = |B| \cos(2\pi 60t + \angle B) = \operatorname{Re}\{B e^{j2\pi 60t}\} \quad B = |B| e^{j\angle B} \\
 & 480\sqrt{2} e^{-j90^\circ} e^{j2\pi 60t} = B e^{j2\pi 60t} + L \frac{d}{dt} (B e^{j2\pi 60t}) \\
 & e^{j2\pi 60t} 480\sqrt{2} e^{-j90^\circ} = B e^{j2\pi 60t} (1 + j2\pi 60L) \\
 & \frac{V_s}{R} = \frac{480\sqrt{2} e^{-j90^\circ}}{0.1 + j23.04} = 29.335 A \\
 & 29.335 \cos(120\pi t - 92^\circ)
 \end{aligned}$$

1cc. Entering 0 into t, this was what was found.

```

% PROJECT 1
% part C
clear all
% values for circuit
Ls = 0.0045;
R1s = 0.1;
R2 = 23.04;
phi = deg2rad(90);

% finding time variables
omega = 2*pi*60;
delta_t = 2*pi/(100*omega);
tau = Ls/(R1s);

t = [0:delta_t:7*tau];

B = (480*sqrt(2))*exp(j*(-phi))/(j*omega*(Ls)+R1s);
B2 = (480*sqrt(2))*exp(j*(-phi))/(j*omega*(Ls)+R1s+R2);

% defining x & y
v_s = (1/(R1s))*480*sqrt(2)*cos(omega*t - phi);
v_c = [];
v_c_0 = abs(B2)*cos(angle(B2));


a = delta_t/tau;
b = (1-(a));

for n = 1:length(t)-1
    if n == 1
        v_c = v_c_0;
    end
    v_c(n+1) = a*v_s(n)+b*v_c(n);
end

figure(2);
plot(t,v_c);
title('Current over time');
xlabel('Time: sec');
ylabel('Current (amps)');

```

1cd. Graph:

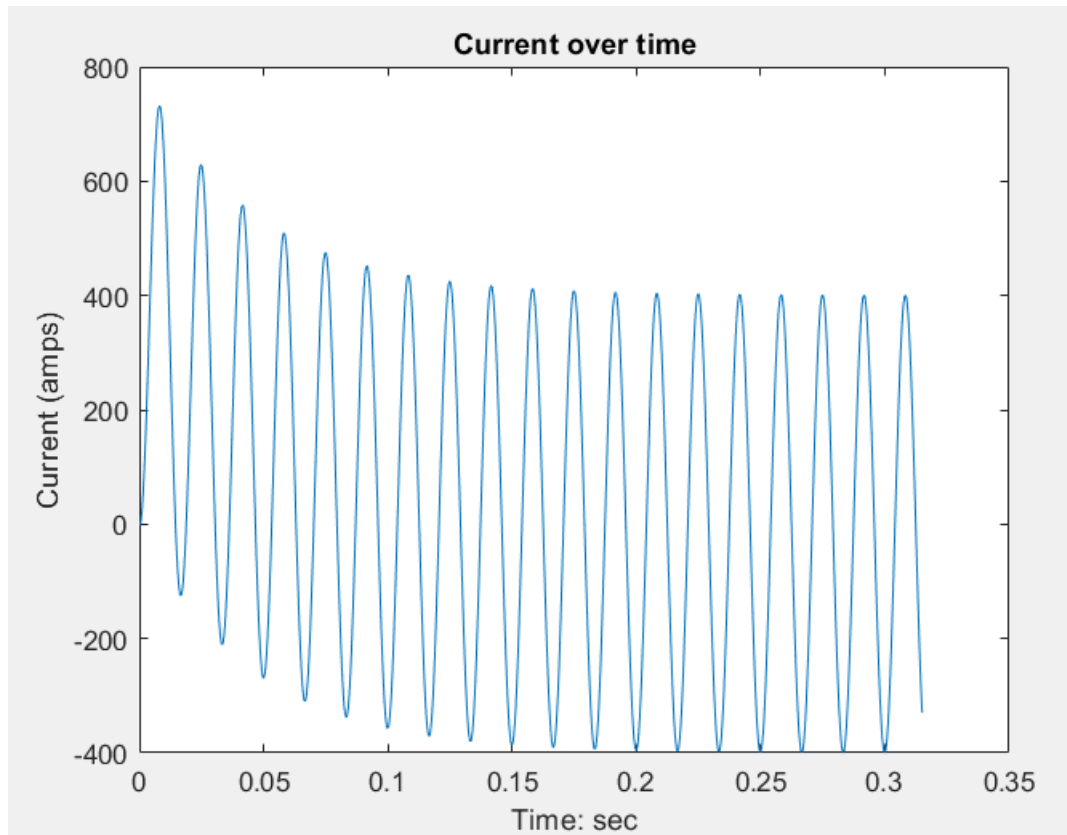

Problem 2 – Audio Filtering

2a & 2b. Write KVL for the loop. Afterwards, write approximation for discretization dx/dt . The discretization for dx/dt is the following:

$$\frac{dx}{dt} \approx \frac{x(n+1) - x(n)}{\Delta t}$$

2a. $-x(t) + V_c + y(t) = 0 \Rightarrow x(t) = \frac{1}{C} \left(\int_0^t dt \right) + Ry(t) \quad \frac{dx}{dt} = y(t) + \frac{d}{dt} \left(\frac{1}{C} \int_0^t dt \right) = \frac{1}{C} + \frac{dy}{dt}$

2b. $y(t + \Delta t) = \frac{\Delta t}{C} x(t) + \left(1 - \frac{\Delta t}{C}\right) y(t) \Rightarrow y(n+1)\Delta t = \frac{\Delta t}{C} x(n) + \left(1 - \frac{\Delta t}{C}\right) y(n)\Delta t$

$y(n+1) = \frac{\Delta t}{C} x(n) + \left(1 - \frac{\Delta t}{C}\right) y(n)$

```

%PROJECT 1
%problem 2
clear all
load('sampleaudio.mat');

%implement given #'s
R = 1;
C = 256.26*10^-6;

tau = R*C;
delta_t = 1/Fs;
A = tau/(tau+delta_t);

t = [0:1:length(x)-1];
y = zeros(size(x));

%plot
for n = 1:1:length(x)-1
    if n == 1
        y(1) = x(1);
    else
        y(n+1) = A * y(n) + A*(x(n+1)-x(n));
    end
end


sound(y,Fs);
subplot(2,1,1)
plot(t, y);
title('Output signal');
xlabel('Time:sec');
ylabel('Voltage');

subplot(2,1,2)
plot(t,x);
title('Input signal');
xlabel('Time:sec');
ylabel('Voltage');

```

2c.

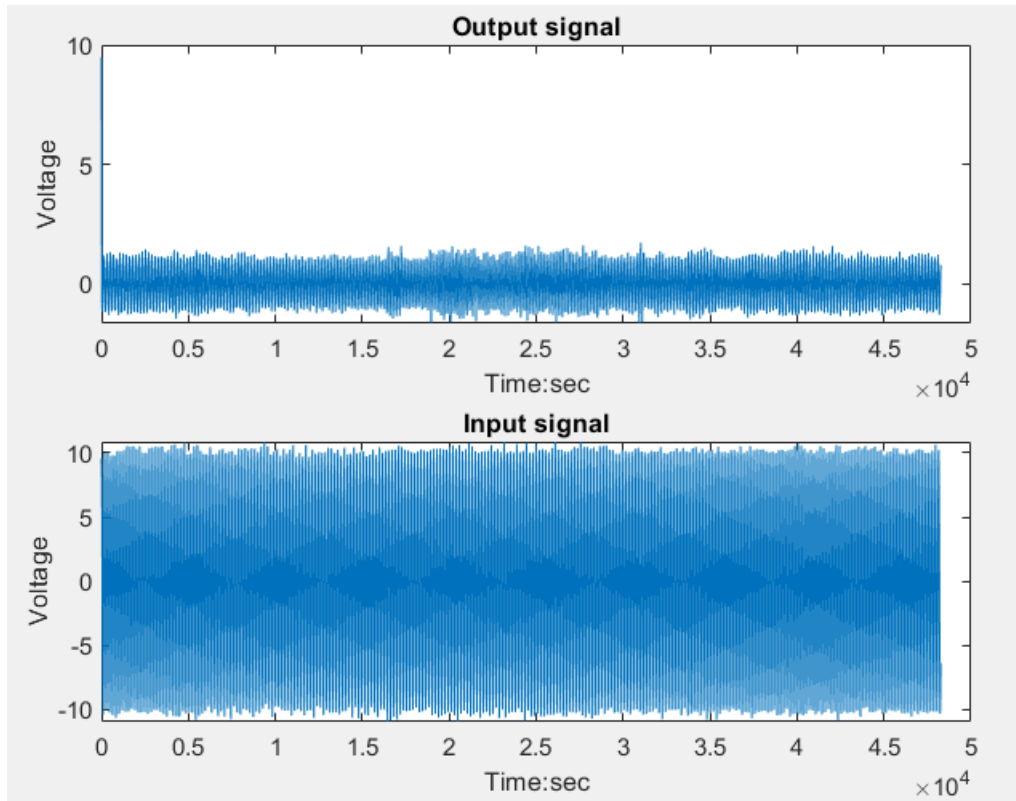2d. The sentence heard was “If only you knew the power of the dark side.”



2e.

Problem 3 – Traditional Communications

3a. Using Euler's identity relationships to figure out how to implement the demodulator, the following steps were done:

$$\begin{aligned}
 3a. \quad x(t) &= [x_{\text{audio}}(t) \cos(2\pi ft)] [\cos(2\pi ft)] \Rightarrow \\
 &\left(\frac{x_{\text{audio}}(t)}{2} e^{j2\pi ft} + \frac{x_{\text{audio}}(t)}{2} e^{-j2\pi ft} \right) \cdot \left(\frac{1}{2} e^{j2\pi ft} + \frac{1}{2} e^{-j2\pi ft} \right) \\
 &= \left(\frac{x_{\text{audio}}(t)}{4} e^{j4\pi ft} + \frac{x_{\text{audio}}(t)}{4} e^{-j4\pi ft} + \frac{x_{\text{audio}}(t)}{2} \right) \\
 &= \frac{x_{\text{audio}}}{2} \left(\frac{1}{2} e^{j4\pi ft} + \frac{1}{2} e^{-j4\pi ft} + 1 \right) = \frac{x_{\text{audio}}(t)}{2} (\cos(4\pi ft) + 1) \\
 \Rightarrow &\frac{1}{2} x_{\text{audio}}(t) + \frac{1}{2} x_{\text{audio}}(t) \cos(4\pi ft)
 \end{aligned}$$

3ba. Setup Code:


```
%PROJECT 1
%Problem 3
clear all

fileID = fopen('problem3.bin', 'r');
x=fread(fileID,'single');
fclose(fileID);
```

3bb. Implementation Code: (Δt_1 and Δt_2 is $n = t/\Delta t$)

```
f = 50*10^3;
fsamp = 2.205 * 10^6;
delta_t = 1/fsamp;
x = x';

delta_t1 = 10.5/delta_t;
delta_t2 = 10.6/delta_t;

t = (0:delta_t:(length(x)-1)*delta_t);
vector = cos(2*pi*f.*t);
x_out = x.*vector;
time = t(delta_t2:88+delta_t2);



figure(1)
subplot(2,1,1);
plot( t(delta_t1:delta_t2) , x(delta_t1:delta_t2) );
title('Graph of x_t');
xlabel('Time: (sec)');
ylabel('Voltage (Volts)');

subplot(2,1,2);
plot( t(delta_t1:delta_t2) , x_out(delta_t1:delta_t2) );
title('Graph of x_out(t)');
xlabel('Time: (sec)');
ylabel('Voltage (Volts)');

figure(2)
subplot(2,1,1)
plot( time, x(delta_t2:88+delta_t2) );
title('Graph of "x_t"');
xlabel('Time: (sec)');
ylabel('Voltage (Volts)');

subplot(2,1,2);
plot( time, x_out(delta_t2:88+delta_t2) );
title('Graph of x_out(t)');
xlabel('Time: (sec)');
ylabel('Voltage (Volts)');
```

3bc. Graph 1:

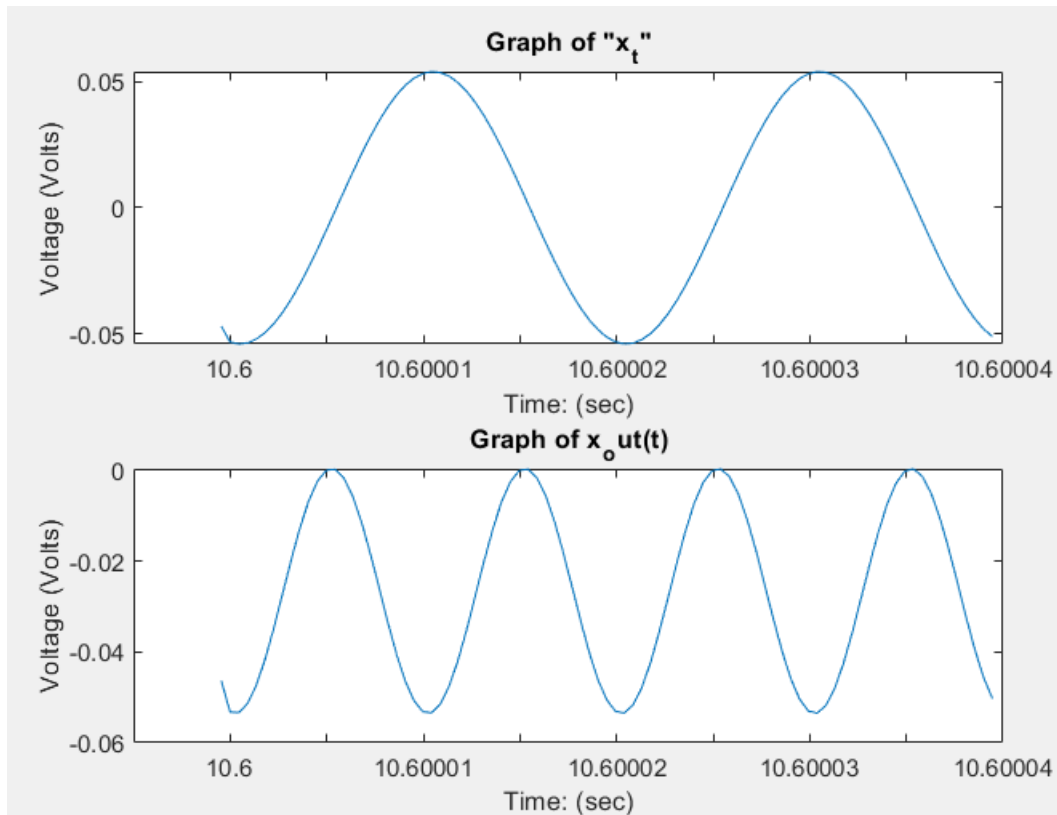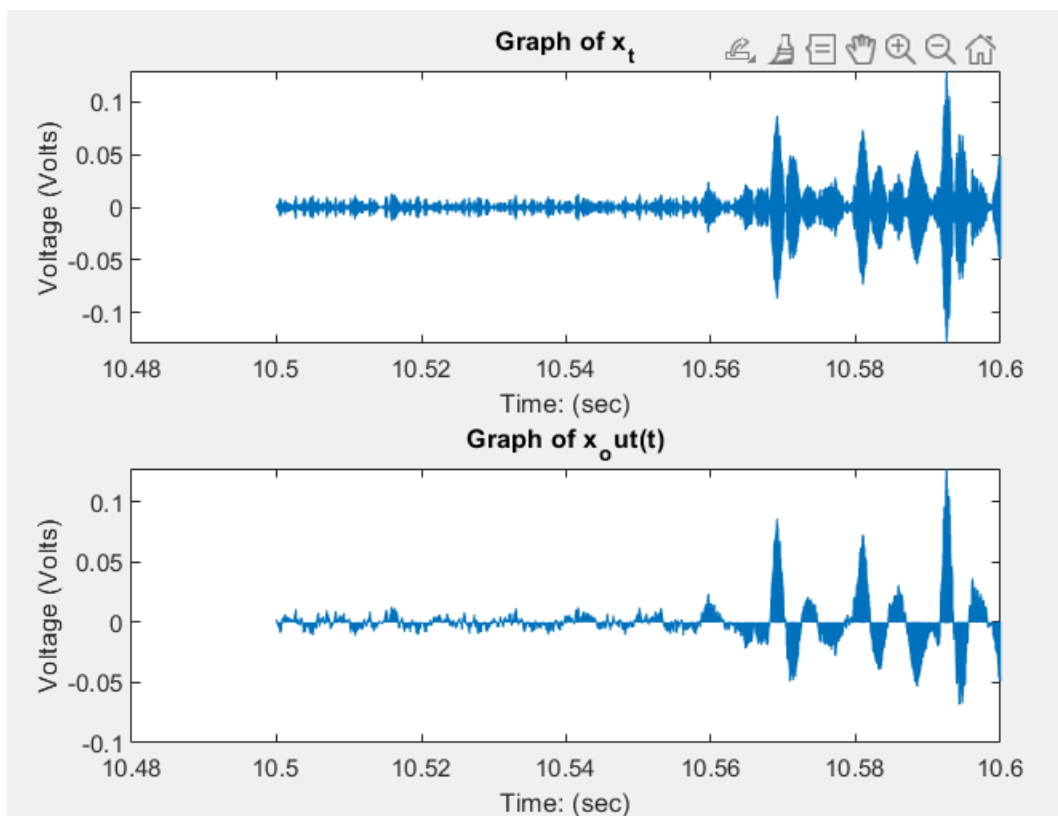

3bd.

3ca. The amplitude from the signal varies because of amplitude modulation.

3cb. When working $X_{out}(t)$, what was noticed was that the frequency of $X_{out}(t)$ should be twice of the input $x(t)$. This is due to the coefficient of $\pi*f*t$ was changed input \rightarrow output.

3da & 3db. Making the differential equation and discrete-time equation:

3d. $i = i_R + i_C \dots i_R = \frac{v(t)}{R}$ & $i_C = C \frac{dv(t)}{dt} \Rightarrow \frac{di}{dt} = \frac{1}{R} \frac{dv(t)}{dt} + C \frac{d^2v(t)}{dt^2}$
 Then loop equation is made: $X_{out}(t) = L \frac{di}{dt} + v(t)$
 $X_{out}(t) = L \left(\frac{1}{R} \frac{dv(t)}{dt} + C \frac{d^2v(t)}{dt^2} \right) + v(t) \Rightarrow \frac{dX_{out}(t)}{dt} = \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{1}{LC} X_{in}(t)$

3dc. Code: (nstart and nend is (seconds*fsamp))

```
%constants for network
R = 28.135;
L = 1.61*10^-3;
C = 1*10^-6;
y0 = 0;
dy0 = 0;
c_1 = 1/(L*C);
c_2 = 1/(R*C);

x_out = x_out/(L*C);
y_1 = zeros(size(t));
y_2 = zeros(size(t));


for n = 1:length(t)-1
    if n == 1
        y_1(1) = y0;
        y_2(1) = dy0;
    end
    y_1(n+1) = y_1(n)+delta_t*y_2(n);
    y_2(n+1) = delta_t*(x_out(n)-c_2*y_2(n)-c_1*y_1(n))+y_2(n);
end

nstart = 10.58*fsamp;
nend = 10.586*fsamp;

newplot = t(nstart:nend); %%10.58*fsamp <-> 10.586*fsamp
figure(3);
subplot(3,1,1);
plot(newplot,2*y_1(nstart:nend))
title('2y_1');

subplot(3,1,2);
plot(newplot,x_out(nstart:nend))
title('x_out');
subplot(3,1,3);
plot(newplot,x(nstart:nend))
title('x');
```

3dd. Graphs:

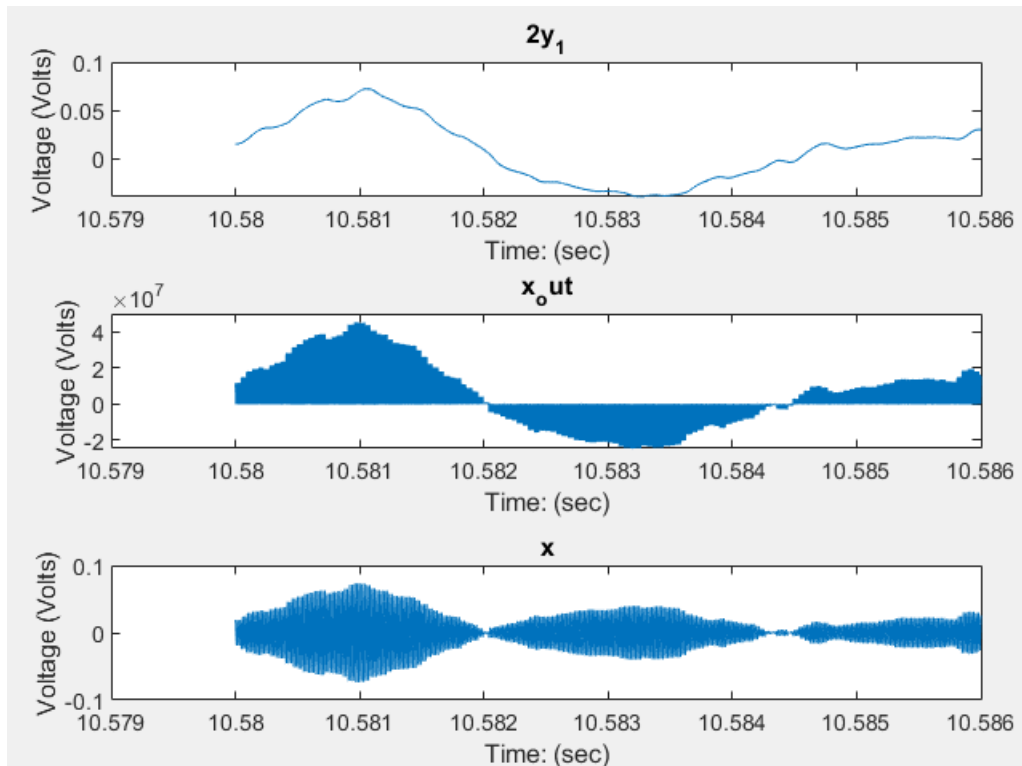

3ea. What happened to the $\cos(4\pi f t)$ by passing $x_{out}(t)$ through the filter was that it was multiplied by $\cos(4\pi f t)$.

3eb. $2y(t)$ appears to relate to $x(t)$ since $x(t)$ is the input that contains the original audio going through the filter that has the carrier cosine wave. $Y(t)$ is what has passed through the filter, where it is the original audio signal with no carrier wave. $Y(t)$ is the amplitude of the input wave.

3f. What plays is a sample recording of the Gettysburg address. X_{out} is noisier than the result because the volume of the output signal was cut in half.

Problem 4 – Complex Communications

4a. $x_3(t)$ would be equal to $e^{(-j*2\pi f t)}$ because it eliminates $e^{(j*2\pi f t)}$ in $x(t)$.

```

%PROJECT 1
%Problem 4
clear all

fileID = fopen('problem4.bin', 'r');
x_in = fread(fileID, 'single');
fclose(fileID);

for n = 2:2:length(x_in)
    x(n/2) = x_in(n-1) + j*x_in(n);
end

%done
f = 50*10^3;
fsamp = 2.205 * 10^6;
delta_t = 1/fsamp;

t = (0:delta_t:(length(x)-1)*delta_t);

x3 = exp(-2*j*pi*f.*t);

xout = x3 .* x;

x1 = real(xout);
x2 = imag(xout);
sound(downsample(x1,100),fsamp/100); %light
sound(downsample(x2,100),fsamp/100); %dark

```

4b.

4c. The light part is the Star Wars main title theme and the dark part is the Imperial March.

Problem 5 – DC Motor Control

5a. Do KVL.

$$5a. -V_a(t) + R_a + L_a \frac{di}{dt} + K \omega(t) = 0 \quad V_a(t) = R i + L \frac{di}{dt} + K \omega(t) \quad \frac{di}{dt} + \frac{R}{L} i = \frac{V_a - K \omega(t)}{L}$$

5b. Using approximation of di/dt and $d(\omega)/dt$, electrical and mechanical discrete time equations turn out to be:

5b.
$$\frac{di}{dt} \approx \frac{i(t+\Delta t) - i(t)}{\Delta t} \approx \frac{\lambda(t+\Delta t) - \lambda(t)}{\Delta t}$$

$$\frac{i(t+\Delta t) - i(t)}{\Delta t} + \frac{R}{L} i = \frac{V_a - K \lambda(t)}{L} \Rightarrow \frac{i(t+\Delta t) - i(t)}{\Delta t} = \frac{V_a - K \lambda(t)}{L} - \frac{R}{L} i$$

electrical: $i(t+\Delta t) - i(t) = \Delta t \left[\frac{V_a - K \lambda(t)}{L} - \frac{R}{L} i \right] \Rightarrow i(t+\Delta t) = \Delta t \left[\frac{V_a - K \lambda(t)}{L} - \frac{R}{L} i \right] + i(t)$

$$\frac{d\lambda}{dt} = \frac{K i_a - B \lambda}{J} \Rightarrow \frac{\lambda(t+\Delta t) - \lambda(t)}{\Delta t} = \frac{K i_a - B \lambda}{J}$$

after algebra...

mechanical: $\lambda(t+\Delta t) = \Delta t \left[\frac{K i_a - B \lambda(t)}{J} \right] + \lambda(t)$

5c. Finding tau and delta_t, the following was calculated for electrical and mechanical:

5c. electrical: $\tau = \frac{L}{R} = \frac{0.01}{5.38} = 2.759 \cdot 10^{-3}$ $\Delta t = \frac{5\tau}{100} = 1.4795 \cdot 10^{-4}$

mechanical: $\tau = \frac{J}{B} = \frac{2 \cdot 10^{-4}}{5 \cdot 10^{-6}} = 40$ $\Delta t = \frac{5\tau}{100} = 2$

To choose which delta_t to use, the smaller value for delta_t was chosen in order to see the full characteristics in the system.

5d. Code:

```

%PROJECT 1
%Problem 5 part d
clear all
L = 0.01;
R = 3.38;
K = 0.029; % motor constant
J = 2*10^-4; % moment of inertia
B = 0.5*10^-5; % damping ratio

tau = L/R;
tauint = 5;
dt = 5*tau/100;
t = 0:dt:tauint;

va = 10;

ia = zeros(size(t));
om = zeros(size(t));


for n = 1:length(t)-1
    if n == 1
        ia(1) = 0;
        om(1) = 0;
        th(1) = 0;
    end
    ia(n+1) = (dt/L)*(va-R*ia(n)-K*om(n))+ia(n);
    om(n+1) = dt*((K/J)*ia(n)-(B/J)*om(n))+om(n);
end

subplot(2,1,1)
plot(t, ia);
title('Current');
xlabel('Time:sec');
ylabel('Amps');

subplot(2,1,2)
plot(t, om);
title('Motor speed');
xlabel('Time:sec');
ylabel('Speed (rad/sec)');

```

Results:

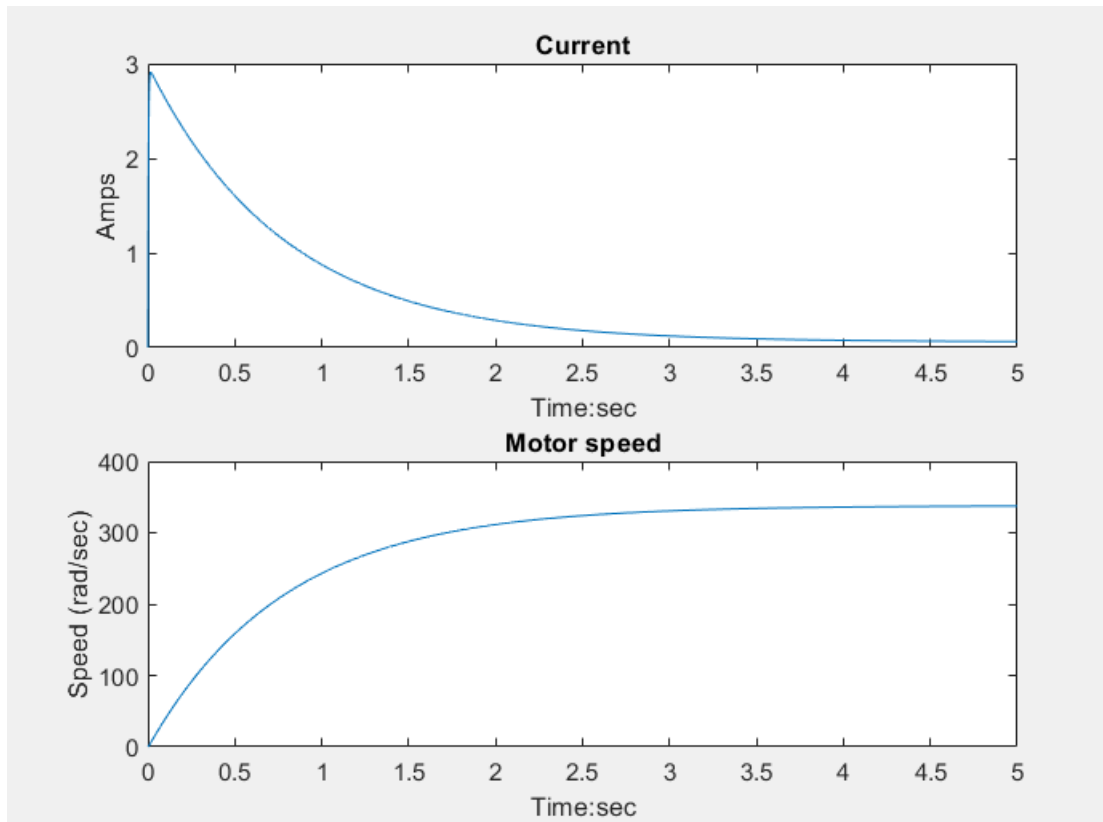

5e. Code: (another for loop was added)


```

for n = 1:1:length(t)-1
    if n == 1
        ia(1) = 0; % current
        om(1) = 0; % motor speed
        th(1) = 0; % motor position
    end
    ia(n+1) = (dt/L)*(va-R*ia(n)-K*om(n))+ia(n); % current
    om(n+1) = dt*((K/J)*ia(n)-(B/J)*om(n))+om(n); % motor speed
    th(n+1) = dt*om(n) + th(n); % motor position
end

for n = 1:1:length(t)-1
    if th(n) >= pi/4
        ia(n+1) = 0;
        om(n+1) = 0;
        th(n+1) = th(n);
    end
end
end

```

Graphs:

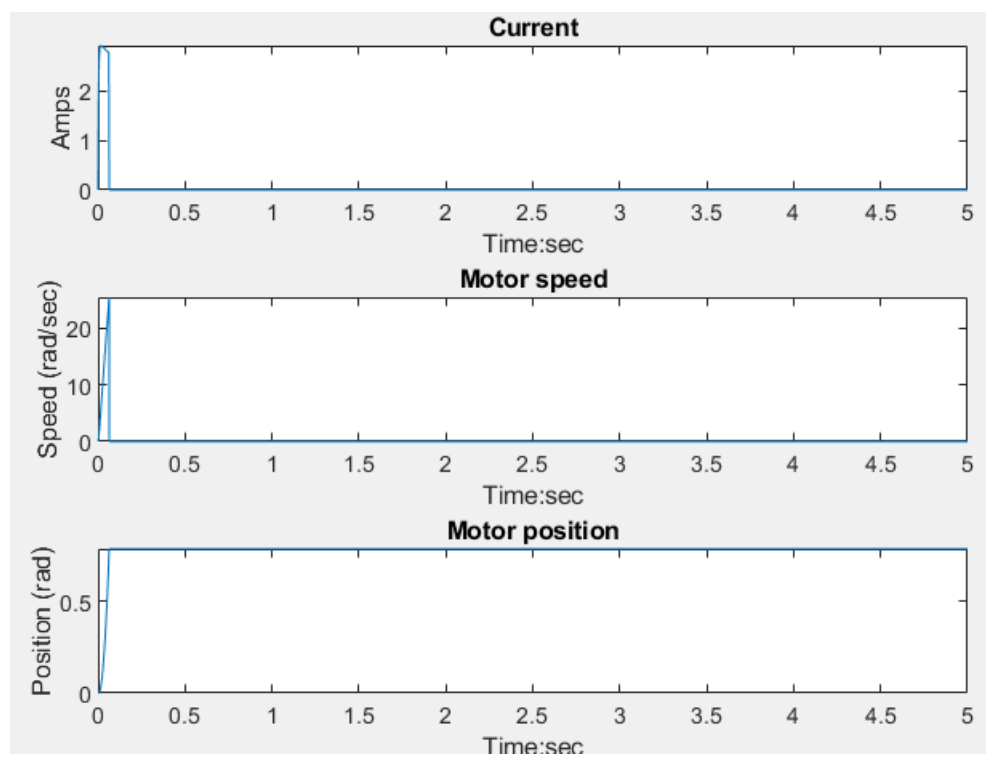

```

%PROJECT 1
%Problem 5 part d
clear all
L = 0.01;
R = 3.38;
K = 0.029; % motor constant
J = 2*10^-4; % moment of inertia
B = 0.5*10^-5; % damping ratio

tau = L/R;
tauint = 5;
dt = 5*tau/100;
t = 0:dt:tauint;

va = 10;

ia = zeros(size(t)); % current
om = zeros(size(t)); % motor speed
th = zeros(size(t)); % motor position

for n = 1:length(t)-1
    if n == 1
        ia(1) = 0; % current
        om(1) = 0; % motor speed
        th(1) = 0; % motor position
    end
    ia(n+1) = (dt/L)*(va-R*ia(n)-K*om(n))+ia(n); % current
    om(n+1) = dt*((K/J)*ia(n)-(B/J)*om(n))+om(n); % motor speed
    th(n+1) = dt*om(n) + th(n); % motor position
end

subplot(3,1,1)
plot(t, ia);
title('Current');
xlabel('Time:sec');
ylabel('Amps');

subplot(3,1,2)
plot(t, om);
title('Motor speed');
xlabel('Time:sec');
ylabel('Speed (rad/sec)');

subplot(3,1,3)
plot(t, th);
title('Motor position');
xlabel('Time:sec');
ylabel('Position (rad)');

```

